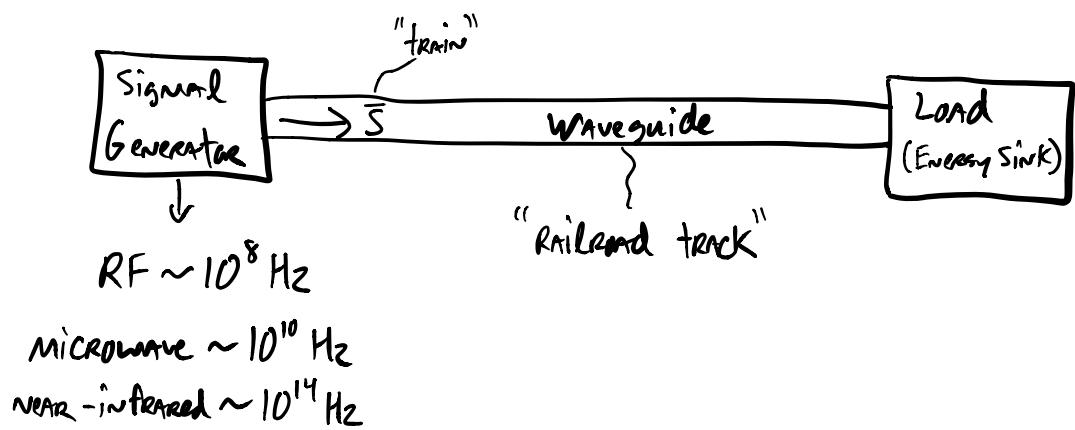


Waveguides

- Guide E+M energy (Poynting vector)
through a structure



Two-Conductor Transmission Lines

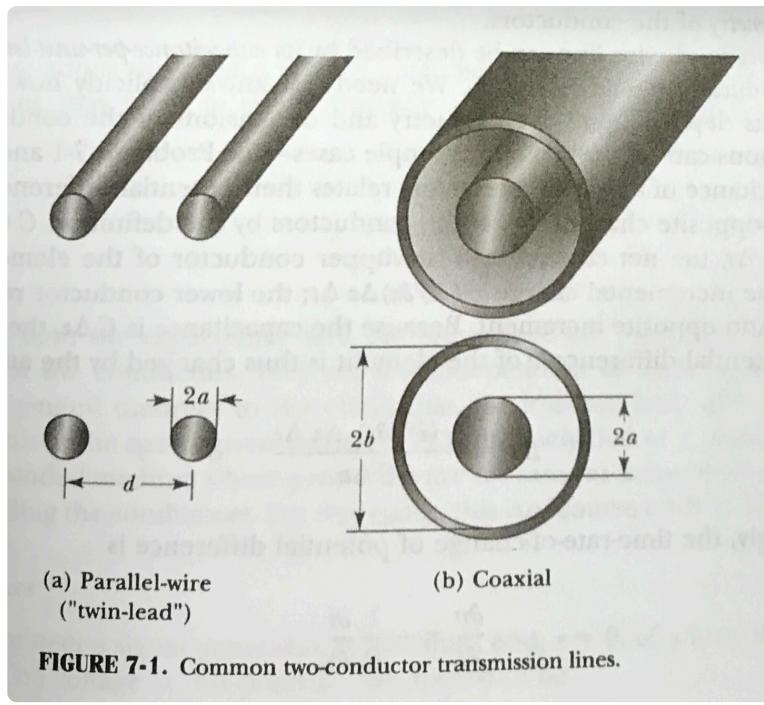



FIGURE 7-1. Common two-conductor transmission lines.

Consider two conductors extending to ∞ in \hat{e}_z as in Figure Above

- Resistance = ρ

- In free space

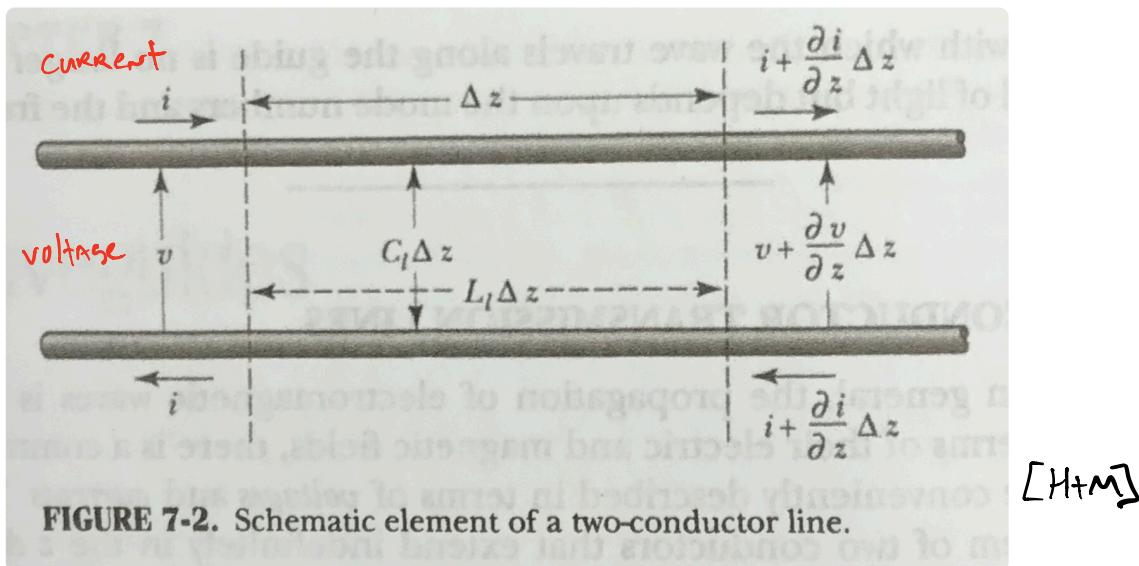Analyzing the behavior in terms of voltage and current



We can calculate the

- Capacitance per unit length, C_e
 - Inductance per unit length, L_l
- } Functions of geometry

The capacitance is defined by

$$C = \frac{q}{v}$$

+ q
 —————
 - v

— charge
 — voltage (potential)

For the top line, the net current is

$$\frac{dq}{dt} = I - \underbrace{I + \frac{\partial I}{\partial z} \Delta z}_{\text{Right}} = - \frac{\partial I}{\partial z} \Delta z$$

left Right

Removes charge Δq from Δz

$$\Rightarrow \Delta q = \frac{\partial I}{\partial z} \Delta z \Delta t$$

↳ "extra" charge delivered

$$\Rightarrow C_L \Delta z = \frac{\Delta q}{\Delta V} = - \frac{\frac{\partial I}{\partial z} \Delta z \Delta t}{\Delta V}$$

$\frac{\partial C}{\partial z}$

$$\Rightarrow \frac{\Delta V}{\Delta t} = - \frac{1}{C_L} \frac{\partial I}{\partial z} \Rightarrow \frac{\partial V}{\partial t} = - \frac{1}{C_L} \frac{\partial I}{\partial z}$$

↳ time rate of change of potential

The self-inductance L relates an induced EMF

to $\frac{\partial I}{\partial t}$:

$$L \equiv \frac{-\text{EMF}}{\frac{\partial I}{\partial t}}$$

The induced EMF across an element Δz :

$$\frac{\partial V}{\partial z} \Delta z = -L_x \Delta z \frac{\partial I}{\partial t}$$

↑
 $L/\Delta z$

$$\Rightarrow \frac{\partial I}{\partial t} = -\frac{1}{L_x} \frac{\partial V}{\partial z}$$

Combining the two equations:

$$\frac{\partial V}{\partial t} = \frac{-1}{C_x} \frac{\partial I}{\partial z} \Rightarrow \frac{\partial^2 V}{\partial t^2} = \frac{-1}{C_x} \frac{\partial^2 I}{\partial z \partial t} \Rightarrow \frac{\partial^2 V}{\partial z \partial t} = \frac{-1}{C_x} \frac{\partial^2 I}{\partial z^2}$$

$$\frac{\partial I}{\partial t} = -\frac{1}{L_x} \frac{\partial V}{\partial z} \Rightarrow \frac{\partial^2 I}{\partial t^2} = -\frac{1}{L_x} \frac{\partial^2 V}{\partial z \partial t} \Rightarrow \frac{\partial^2 I}{\partial z \partial t} = -\frac{1}{L_x} \frac{\partial^2 V}{\partial z^2}$$

$$\Rightarrow \frac{\partial^2 V}{\partial t^2} = \frac{1}{C_e L_e} \frac{\partial^2 V}{\partial z^2}$$

$$\frac{\partial^2 I}{\partial t^2} = \frac{1}{C_e L_e} \frac{\partial^2 I}{\partial z^2}$$


$$\Rightarrow \begin{cases} \frac{\partial^2 V}{\partial z^2} + C_e L_e \frac{\partial^2 V}{\partial t^2} = 0 \\ \frac{\partial^2 I}{\partial z^2} + C_e L_e \frac{\partial^2 I}{\partial t^2} = 0 \end{cases}$$

Look familiar?
wave equations!

$$\text{wave speed} \Rightarrow c = \frac{1}{\sqrt{L_e C_e}}$$

- C_e and L_e depend on geometry but are dependent on each other.
- For loss-free lines with constant cross-section,
 $c = \text{speed of plane wave} = 3 \times 10^8 \text{ cm/s}$ in free space

Impedances

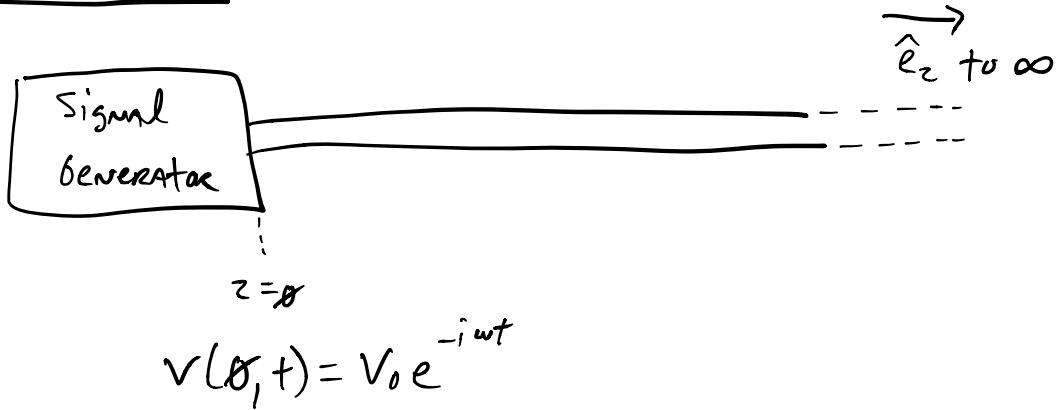

NO return signal so

$$v(z, t) = V_0 e^{i(kz - \omega t)}$$

\hookrightarrow solution to wave eqn

In-class Problem:

Calculate $I(z, t)$ from $v(z, t)$

Solution

$$\frac{\partial I}{\partial t} = -\frac{1}{L_e} \frac{\partial V}{\partial z} \Rightarrow I = \frac{-ik}{L_e} \int V_0 e^{i(kz-wt)} dt$$

$$\Rightarrow I = \frac{k}{w} \frac{V_0}{L_e} e^{i(kz-wt)} = \frac{1}{c} \frac{V_0}{L_e} e^{i(kz-wt)}$$


But $c = \frac{1}{\sqrt{L_e C_e}}$ $\Rightarrow I(z, t) = \frac{1}{\sqrt{\frac{C_e}{L_e}}} V_0 e^{i(kz-wt)}$

\Rightarrow The current is in phase with the voltage

The characteristic impedance Z_0 is defined by:

$$Z_0 \equiv \frac{V}{I} = \sqrt{\frac{L_e}{C_e}} \quad (\text{Think } V=IR)$$

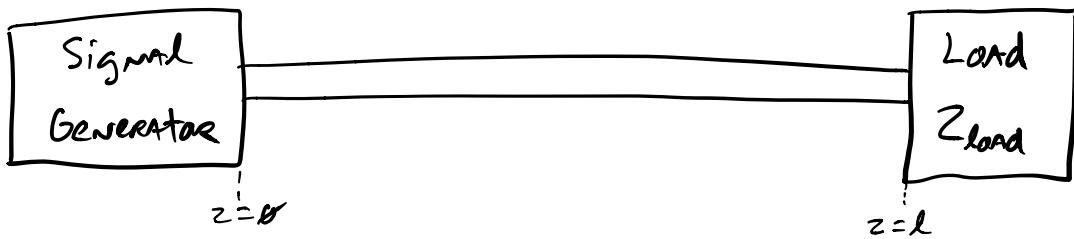For a lossless line, $Z_0 = \text{Resistance}$, and is independent of frequency



- If $Z_{load} = Z_0 = \sqrt{\frac{L}{C}}$ no wave is reflected and the line transfers power from the signal generator to the load
- If $Z_{load} \neq Z_0$, there is an impedance mismatch and the wave is partially reflected
 \Rightarrow standing wave is produced

Superposition of \rightarrow and \leftarrow waves

$$V(z, t) = V_+ e^{i(kz - \omega t)} + V_- e^{i(-kz - \omega t)}$$

$$I(z, t) = I_+ e^{i(kz - \omega t)} + I_- e^{i(-kz - \omega t)}$$

The load impedance at $z=l$:

$$Z_{\text{load}} = \frac{V(l,t)}{I(l,t)} = \frac{V_+ e^{ikl} + V_- e^{-ikl}}{I_+ e^{ikl} + I_- e^{-ikl}}$$

Note: In general, the impedance is complex

with $Z = R - iX$

$\begin{matrix} | & \\ \text{resistance} & \text{reactance} \end{matrix}$

(Electrical Engineer notation $Z = R + iX$)
 $\angle_{\text{from}} e^{+i\omega t}$

The \rightarrow and \leftarrow voltages and currents obey

$$\frac{V_+}{I_+} = -\frac{V_-}{I_-} = Z_0$$


The generator (input) impedance is

$$Z_{\text{gen}} \equiv \frac{V(0,t)}{I(0,t)} = \frac{V_+ + V_-}{I_+ + I_-}$$

Comparing Z_{load} , Z_{gen} , and Z_0 we find

$$Z_{gen} = Z_0 \frac{Z_{load} - iZ_0 \tan kl}{Z_0 + iZ_{load} \tan kl}$$

- provides complex impedance as a fn of load impedance Z_{load} , characteristic impedance Z_0 , and distance l
- Z_{gen} is periodic wrt l

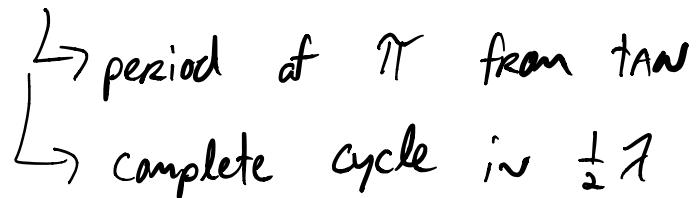
 period of π from tan
 complete cycle in $\pm \frac{\pi}{2}$

The amplitude of reflection is

$$r \equiv \frac{V_- e^{-ikl}}{V_+ e^{ikl}} = \frac{Z_{load} - Z_0}{Z_{load} + Z_0}$$

Power reflection coef:

$$R = \left| \frac{Z_{load} - Z_0}{Z_{load} + Z_0} \right|^2$$

- r and R are analogs of plane wave reflection from an interface for normal incidence
- As $\omega \rightarrow 0, \tau \rightarrow \infty$ (low frequency)
the properties reduce to elementary circuit theory ($V=IR$, Kirchhoff's rules)